

Induction Motor - I_{dr} Full Derivation & Stamp

Friday, March 5, 2021 8:20 AM

The voltage equation for the d phase of the rotor in the stationary reference frame:

$$\begin{aligned} v_{dr} &= R_r I_{dr} + p\psi_{dr} - \psi_{qr}\omega_r \\ \psi_{dr} &= (L_{lr} + L_m)I_{dr} + L_m I_{ds} \\ \psi_{qr} &= (L_{lr} + L_m)I_{qr} + L_m I_{qs} \\ L_r &= L_{lr} + L_m \end{aligned}$$

To solve any power grid or circuit element with nonlinearities through time, remember **EDLS**

- **Expand**
- **Discretize**
- **Linearize**
- **Stamp**

1. Step 1 - Expand: Expand the differential algebraic voltage equation.

In our induction motor, the rotor circuit is shorted, so $V_{dr} = 0$

$$\rightarrow 0 = R_r i_{dr}(t) + p(L_m i_{ds}(t) + L_m i_{dr}(t)) - \omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t)) + R_r i_{dr}(t)$$

$$\rightarrow 0 = L_r \frac{\partial i_{dr}(t)}{\partial t} + L_m \frac{\partial i_{ds}(t)}{\partial t} - \omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t)) + R_r i_{dr}(t)$$

$$\rightarrow -R_r i_{dr}(t) = L_r \frac{\partial i_{dr}(t)}{\partial t} + L_m \frac{\partial i_{ds}(t)}{\partial t} - \omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t))$$

$$\rightarrow -R_r i_{dr}(t) + \omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t)) = L_r \frac{\partial i_{dr}(t)}{\partial t} + L_m \frac{\partial i_{ds}(t)}{\partial t}$$

2. Step 2 - Discretize: Apply the trapezoidal rule to eliminate the differential terms and obtain an algebraic equation.

First, multiply both sides of the equation by Δt :

$$\rightarrow (-R_r i_{dr}(t) + \omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t))) \Delta t = L_r \frac{\partial i_{dr}(t)}{\partial t} + L_m \frac{\partial i_{ds}(t)}{\partial t}$$

$$\rightarrow \sum_{t}^{t+\Delta t} (-R_r i_{dr}(\tau) + \omega_r(\tau)(L_r i_{qr}(\tau) + L_m i_{qs}(\tau))) \Delta \tau = L_r \frac{\partial i_{dr}(t)}{\partial t} + L_m \frac{\partial i_{ds}(t)}{\partial t}$$

Apply the Trapezoidal Integration approximation:

$$\rightarrow -R_r (i_{dr}(t+\Delta t) + i_{dr}(t)) + [\omega_r(t+\Delta t)(L_r i_{qr}(t+\Delta t) + L_m i_{qs}(t+\Delta t)) + (\omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t)))] = \frac{2L_r}{\Delta t} (i_{dr}(t+\Delta t) - i_{dr}(t)) + \frac{2L_m}{\Delta t} (i_{ds}(t+\Delta t) - i_{ds}(t))$$

$$\rightarrow -R_r i_{dr}(t) + \omega_r(t)(L_r i_{qr}(t) + L_m i_{qs}(t)) = \left(R_r + \frac{2L_r}{\Delta t} \right) i_{dr}(t+\Delta t) + \frac{2L_m}{\Delta t} i_{ds}(t+\Delta t) - \omega_r(t+\Delta t)(L_r i_{qr}(t+\Delta t) + L_m i_{qs}(t+\Delta t)) - \frac{2L_r}{\Delta t} i_{dr}(t) - \frac{2L_m}{\Delta t} i_{ds}(t)$$

$$\rightarrow V_{erdr}(t) + V_{emds}(t) = \left(R_r + \frac{2L_r}{\Delta t} \right) i_{dr}(t+\Delta t) + \frac{2L_m}{\Delta t} i_{ds}(t+\Delta t) - \omega_r(t+\Delta t)(L_r i_{qr}(t+\Delta t) + L_m i_{qs}(t+\Delta t)) - \frac{2L_r}{\Delta t} i_{dr}(t) - \frac{2L_m}{\Delta t} i_{ds}(t)$$

$$\rightarrow O = \left(R_r + \frac{2L_r}{\Delta t} \right) i_{dr}(t+\Delta t) + \frac{2L_m}{\Delta t} i_{ds}(t+\Delta t) - \omega_r(t+\Delta t)(L_r i_{qr}(t+\Delta t) + L_m i_{qs}(t+\Delta t)) + hist_{dr}(t)$$

$$\text{where } hist_{dr}(t) = -V_{erdr}(t) - V_{emds}(t) \rightarrow \frac{2L_r}{\Delta t} i_{dr}(t) - \frac{2L_m}{\Delta t} i_{ds}(t)$$

3. **Step 3 - Linearize:** Perform a 1st order Taylor Expansion to linearize your entire nonlinear algebraic equation.

$$f^{k+1} \approx f^k + f'(x^k) \cdot (x^{k+1} - x^k)$$


$$\begin{aligned} f_{dr}^k(I_{dr}^k(t+\Delta t), I_{ds}^k(t+\Delta t), w_r^k(t+\Delta t), I_{qr}^k(t+\Delta t), I_{qs}^k(t+\Delta t)) &= \left(R_{dr} + \frac{2L_r}{\Delta t} \right) i_{dr}(t+\Delta t) + \frac{2L_m}{\Delta t} i_{ds}(t+\Delta t) - w_r(t+\Delta t) (L_r i_{qr}(t+\Delta t) + L_m i_{qs}(t+\Delta t)) + h_{int_dr}(t) \\ \rightarrow f_{dr}^{k+1}(I_{dr}^{k+1}(t+\Delta t), I_{ds}^{k+1}(t+\Delta t), w_r^{k+1}(t+\Delta t), I_{qr}^{k+1}(t+\Delta t), I_{qs}^{k+1}(t+\Delta t)) &= \underbrace{f_{dr}^k(I_{dr}^k(t+\Delta t), I_{ds}^k(t+\Delta t), w_r^k(t+\Delta t), I_{qr}^k(t+\Delta t), I_{qs}^k(t+\Delta t))}_{f_{dr}^k} \\ &\quad + \frac{\partial f_{dr}}{\partial I_{dr}} (I_{dr}^{k+1}(t+\Delta t) - I_{dr}^k(t+\Delta t)) \\ &\quad + \frac{\partial f_{dr}}{\partial I_{ds}} (I_{ds}^{k+1}(t+\Delta t) - I_{ds}^k(t+\Delta t)) \\ &\quad + \frac{\partial f_{dr}}{\partial I_{qr}} \Big|_{w_r^k} (I_{qr}^{k+1}(t+\Delta t) - I_{qr}^k(t+\Delta t)) \\ &\quad + \frac{\partial f_{dr}}{\partial I_{qs}} \Big|_{w_r^k} (I_{qs}^{k+1}(t+\Delta t) - I_{qs}^k(t+\Delta t)) \\ &\quad + \frac{\partial f_{dr}}{\partial w_r} \Big|_{I_{qr}^k, I_{qs}^k} (w_r^{k+1}(t+\Delta t) - w_r^k(t+\Delta t)) \end{aligned}$$

4. **Step 4 - Stamp:** Relate linearized equations to circuit elements. Add elements systematically to the Y matrix.

We now have a linearized equation. We must separate our final equation into our knowns (values at iteration k and time $t + \Delta t$ or values just at time t) and unknowns (values at iteration k and time $t + \Delta t$). Rearranging our previous equation and relating our partial derivatives to their corresponding circuit elements we get:

$$\begin{aligned} \rightarrow f_{dr}^{k+1}(I_{dr}^{k+1}(t+\Delta t), I_{ds}^{k+1}(t+\Delta t), w_r^{k+1}(t+\Delta t), I_{qr}^{k+1}(t+\Delta t), I_{qs}^{k+1}(t+\Delta t)) &= \frac{\partial f_{dr}}{\partial I_{dr}} (I_{dr}^{k+1}(t+\Delta t)) \xrightarrow{\text{Resistance}} R_{dr} \\ &\quad + \frac{\partial f_{dr}}{\partial I_{ds}} (I_{ds}^{k+1}(t+\Delta t)) \xrightarrow{\text{Current Controlled Voltage Source}} R_{ds} I_{ds}^{k+1}(t+\Delta t) \\ &\quad + \frac{\partial f_{dr}}{\partial I_{qr}} \Big|_{w_r^k} (I_{qr}^{k+1}(t+\Delta t)) \xrightarrow{\text{Voltage Controlled Current Source}} R_{qr} I_{qr}^{k+1}(t+\Delta t) \\ &\quad + \frac{\partial f_{dr}}{\partial I_{qs}} \Big|_{w_r^k} (I_{qs}^{k+1}(t+\Delta t)) \xrightarrow{\text{Voltage Controlled Current Source}} R_{qs} I_{qs}^{k+1}(t+\Delta t) \\ &\quad + \frac{\partial f_{dr}}{\partial w_r} \Big|_{I_{qr}^k, I_{qs}^k} (w_r^{k+1}(t+\Delta t)) \xrightarrow{\text{Voltage Controlled Voltage Source}} R_w \\ &\quad + f_{dr}^k - \frac{\partial f_{dr}}{\partial I_{dr}} (I_{dr}^k(t+\Delta t)) \\ &\quad - \frac{\partial f_{dr}}{\partial I_{ds}} (I_{ds}^k(t+\Delta t)) \\ &\quad - \frac{\partial f_{dr}}{\partial I_{qr}} \Big|_{w_r^k} (I_{qr}^k(t+\Delta t)) \\ &\quad - \frac{\partial f_{dr}}{\partial I_{qs}} \Big|_{w_r^k} (I_{qs}^k(t+\Delta t)) \\ &\quad - \frac{\partial f_{dr}}{\partial w_r} \Big|_{I_{qr}^k, I_{qs}^k} (w_r^k(t+\Delta t)) \xrightarrow{\text{Independent Voltage Source}} V_{dr, eq} \end{aligned}$$

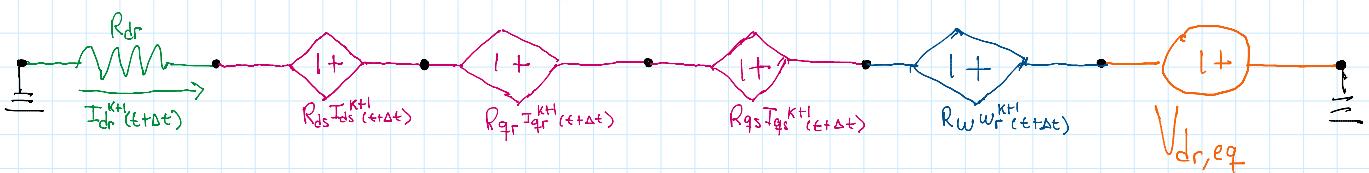From our equations above, we know our final linearized equivalent circuit at $k+1$ that we stamp looks like this:



We can use KVL to stamp the circuit in the matrix. We will stamp each circuit element with respect to its controlling node in the Y matrix which houses all our partial derivatives at iteration $k + 1$ and time $t + \Delta t$. We will stamp our independent voltage source (our known values evaluated at iteration k and time $t + \Delta t$) in J vector. If we look at just the row corresponding to I_{dr} , our equivalent circuit stamps should look like this:

In row I_{dr}^{k+1} of our Y matrix

$$I_{dr} \begin{bmatrix} I_{dr} & I_{ds} & I_{qr} & I_{qs} & w_r \\ R_{dr} & R_{ds} & R_{qr} & R_{qs} & R_w \end{bmatrix}$$

In row I_{dr} of our J Vector

$$I_{dr} \begin{bmatrix} -V_{dr, eq} \end{bmatrix}$$